
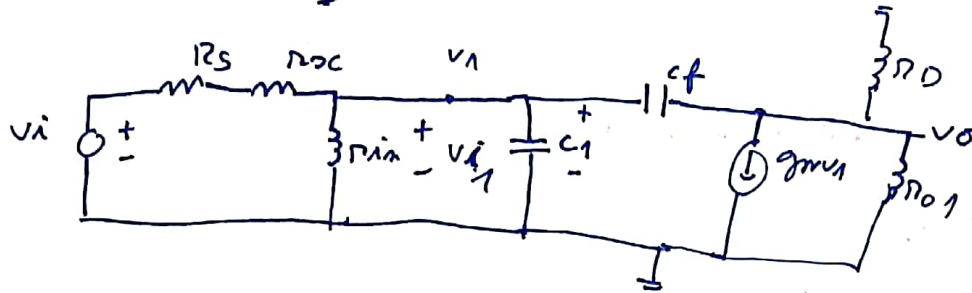


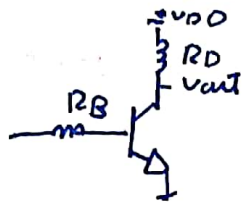Resistive common emitter stage ac ckt analysis



$$Z_1 = R_S + R_{\pi}$$

$$Z_2 = R_D || r_{o1}$$

$$Z_3 = r_{in} || \frac{1}{C_1 s}$$

$$= \frac{r_{in}}{r_{in} C_1 s + 1}$$

at v1

$$\frac{v_1}{Z_3} + \frac{v_1 - v_{in}}{R_S + R_{\pi}} + (v_1 - v_o) C_f s = 0$$

$$v_1 \left(\frac{1}{Z_3} + \frac{1}{R_S + R_{\pi}} + C_f s \right) = \frac{v_{in}}{R_S + R_{\pi}} + v_o C_f s$$

$$v_1 = \frac{\frac{v_{in}}{R_S + R_{\pi}} + v_o C_f s}{\left(\frac{1}{Z_3} + \frac{1}{R_S + R_{\pi}} + C_f s \right)}$$

Sum of currents at v1

$$\frac{v_1}{Z_3} + (v_1 - v_{out}) C_f s + \frac{v_1 - v_{in}}{Z_1} = 0$$

$$v_1 \left(\frac{1}{Z_3} + C_f s + \frac{1}{Z_1} \right) = v_{out} C_f s + \frac{v_{in}}{Z_1} \quad | \quad A_{v(s)} = \frac{-\frac{1}{Z_1}}{\frac{1}{Z_3} + C_f s + \frac{1}{Z_1}}$$

$$v_1 = \frac{v_{out} C_f s + \frac{v_{in}}{Z_1}}{\left(\frac{1}{Z_3} + C_f s + \frac{1}{Z_1} \right)} \quad | \quad \frac{\frac{1}{Z_2} + C_f s + C_f s + \frac{C_f s}{\left(\frac{1}{Z_3} + C_f s + \frac{1}{Z_1} \right)} (g_{m1} - C_f s)}{\left(\frac{1}{Z_3} + C_f s + \frac{1}{Z_1} \right)}$$

Sum of currents at vout

$$\frac{v_{out}}{Z_2} + g_{m1} v_1 + (v_{out} - v_1) C_f s = 0$$

$$v_{out} \left(\frac{1}{Z_2} + C_f s + \frac{C_f s}{\left(\frac{1}{Z_3} + C_f s + \frac{1}{Z_1} \right)} \right) (g_{m1} - C_f s) = -v_{in} \left(\frac{\frac{1}{Z_1}}{\frac{1}{Z_3} + C_f s + \frac{1}{Z_1}} \right)$$

Im Put Impedance

UPL-

$$\text{Impedance In Put} = \text{---} (R_D + R_{DC}) + \frac{r_{in}}{C_{1D} R_{in} + 1}$$

out Put Impedance

at v_1

$$I_x = \frac{v_1}{R_{DCT} + R_D} + \frac{v_1}{Z_3} + (\text{---}) = 0$$

$$\frac{v_1}{R_{DCT} + R_D} + \frac{v_1}{Z_3} + (v_1 - v_{out}) C_{1D} = 0$$

$$\frac{v_{out} C_{1D}}{\frac{1}{Z_1} + \frac{1}{Z_3} + C_{1D}} = v_1$$

$$I_{DC} = \frac{v_{out}}{Z_2} + g_{m1} v_1 + (v_{out} - v_1) C_{1D}$$

$$I_{DC} = v_{out} \left(\frac{1}{Z_2} + \frac{C_{1D}}{\frac{1}{Z_1} + \frac{1}{Z_3} + C_{1D}} \right) + g_{m1} v_1$$


$$\frac{v_{out}}{I_x} = \frac{1}{\left(\frac{1}{Z_2} + C_{1D} + \frac{C_{1D}}{\frac{1}{Z_1} + \frac{1}{Z_3} + C_{1D}} \right) (g_{m1} - C_{1D})}$$

↓
get smaller with frequency

Resistive common emitter stage

Full analysis

DC analysis

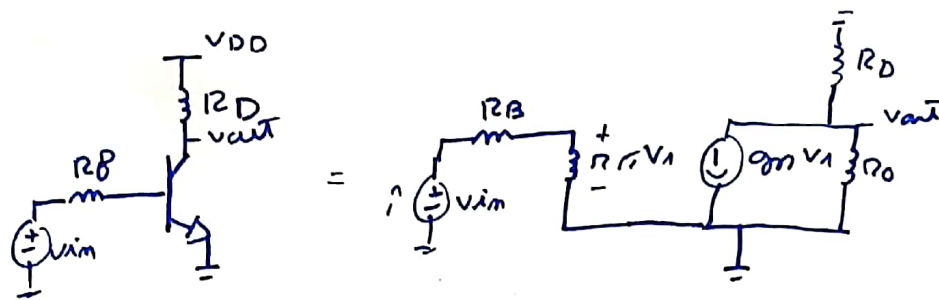

Input Impedance

$$R_{in} = \frac{v_{in}}{I_{in}} = \frac{v_{in}}{I_{B+T}} = I_{in} = \frac{v_{in}}{R_{in}} = \frac{R_B + r_{\pi}}{\text{controlled}}$$

g_m

g_m

$$\frac{v_{in}}{I_{B+T}}$$

$$\frac{I_{out}}{v_{in}}$$

$$v_1 = \frac{r_{\pi}}{R_B + r_{\pi}} v_{in}$$

$$g_m \frac{r_{\pi}}{R_B + r_{\pi}} v_{in} = I_O$$

$$g_m \frac{r_{\pi}}{R_B + r_{\pi}} = \underline{GM} \rightarrow \text{overall gain}$$

↳ only controlled

AV gain

$$v_1 = v_{in} \frac{r_{\pi}}{R_B + r_{\pi}}$$

$$\frac{v_{out}}{R_D} + \frac{v_{out}}{r_o} + g_m v_1 = 0$$

$$v_{out} \left(\frac{1}{R_D} + \frac{1}{r_o} \right) = -v_{in} g_m \frac{r_{\pi}}{R_B + r_{\pi}}$$

$$\frac{v_{out}}{v_{in}} = \frac{-g_m r_{\pi}}{(R_B + r_{\pi}) \times \left(\frac{1}{R_D} + \frac{1}{r_o} \right)} = \frac{-g_m r_{\pi} R_D r_o}{(R_B + r_{\pi})(R_D + r_o)}$$

↑ controlled

↑ controlled

output Impedance

$$R_{o||R_D} = \underline{R_{out}}$$

~~Big~~ large signal analysis

$$I_C \approx I_B \times \beta \quad \text{when } V_{CE} > V_{CEsat}$$

$$V_{CE} = V_{DD} - I_C R_D$$


$$I_B \approx \frac{V_{in} - 0.7}{R_B}$$

~~Knowing the average β value the value of the gain~~

$$I_C = \beta \left(\frac{V_{in} - 0.7}{R_B} \right)$$

$$V_{CE}^{sat} = V_{DD} - \beta \left(\frac{V_{in} - 0.7}{R_B} \right) \times \underbrace{R_D}_{\substack{\text{controls} \\ \text{the gain}}}$$

A - gain

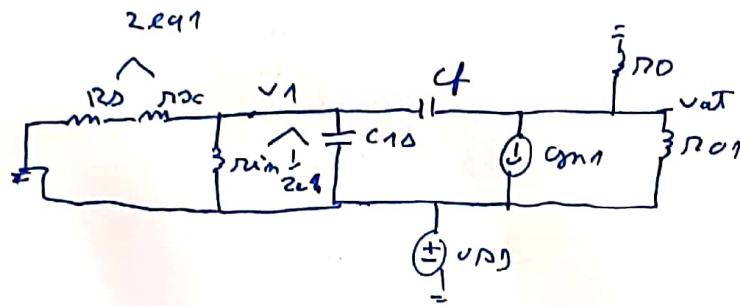

$$Z_{eq2} = \frac{12 \text{ k}\Omega}{R_{in} \text{ cfs} + 1}$$

$$Z_1 = R_D + R_{D1}$$

$$\frac{v_1 - V_{DD}}{R_D Z_{eq1}} + \frac{v_1 - V_{DD}}{Z_{eq2}} + (v_1 - v_{out}) \text{cfs} = 0$$

$$v_1 \left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right) = \frac{V_{DD} \left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} \right) + v_{out} \text{cfs}}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right)}$$

$$\frac{v_{out}}{R_D} + \frac{v_{out} - V_{DD}}{R_{D1}} + g_m v_1 + (v_{out} - v_1) \text{cfs} = 0$$

$$\frac{v_{out}}{R_D} \left(\frac{1}{R_D} + \frac{1}{R_{D1}} + \text{cfs} + \frac{\text{cfs}}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right) (g_m - \text{cfs})} \right) =$$


$$V_{DD} \left(\frac{1}{R_{D1}} + \frac{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} \right)}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right)} \right) (\text{cfs} - g_m)$$

$$\frac{v_{out}}{V_{DD}} = \frac{\left(\frac{1}{R_{D1}} + \frac{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} \right)}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right)} \right) (\text{cfs} - g_m)}{\left(\frac{1}{R_D} + \frac{1}{R_{D1}} + \text{cfs} + \frac{\text{cfs}}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right) (g_m - \text{cfs})} \right)}$$

$$\left(\frac{1}{R_D} + \frac{1}{R_{D1}} + \text{cfs} + \frac{\text{cfs}}{\left(\frac{1}{Z_{eq1}} + \frac{1}{Z_{eq2}} + \text{cfs} \right) (g_m - \text{cfs})} \right)$$

low frequ: \rightarrow decreases with frequency

Δ+ gain

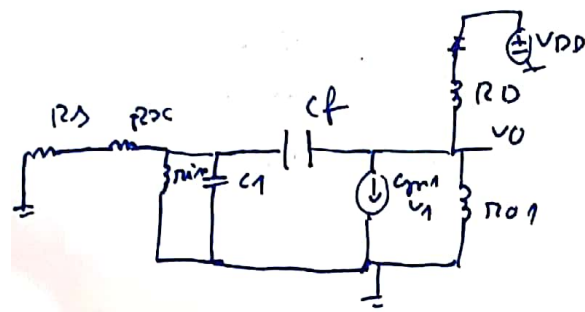

~~$$Z_1 = R_S + R_G$$

$$Z_2 = r_{in} || C_1 || Z_3$$

$$Z_3 = \frac{1}{C_1 s} + Z_2$$~~

~~$$Z_4 = r_{o1} || Z_3$$~~

~~$$Z_1 = R_S + R_G$$~~

~~$$Z_2 = \frac{1}{C_1 s} || r_{in} = \frac{r_{in}}{r_{in} C_1 s + 1}$$~~

sum of currents at V_1

$$\frac{V_1}{Z_1} + \frac{V_1}{Z_2} + (V_1 - V_{out}) C_1 s = 0$$

$$V_1 = \frac{C_1 s}{\frac{1}{Z_1} + \frac{1}{Z_2} + C_1 s} = \frac{1}{\frac{1}{Z_1 C_1 s} + \frac{1}{Z_2 C_1 s} + 1}$$

sum of currents at V_{out}

$$\frac{V_{out}}{r_{o1}} + g_m V_1 + \frac{V_{out} - V_{DD}}{R_D} = 0$$

$$V_{out} \left(\frac{1}{r_{o1}} + \frac{g_m}{\frac{1}{Z_1 C_1 s} + \frac{1}{Z_2 C_1 s} + 1} + \frac{1}{R_D} \right) = \frac{V_{DD}}{R_D}$$

$$\frac{V_{out}}{V_{DD}} = \frac{\frac{1}{R_D}}{\frac{1}{r_{o1}} + \frac{g_m}{\frac{1}{Z_1 C_1 s} + \frac{1}{Z_2 C_1 s} + 1}}$$

$Z_1 \rightarrow \text{const}$

$Z_2 \rightarrow \text{decreases with frequency}$

\rightarrow at low frequency

$\frac{1}{r_{o1}} \rightarrow \text{only}$

\rightarrow decreases with frequency

$$\frac{1}{r_{o1}} + \frac{g_m}{Z_1}$$