
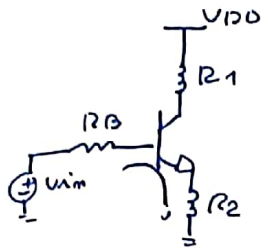


# Degenerated Source Follower

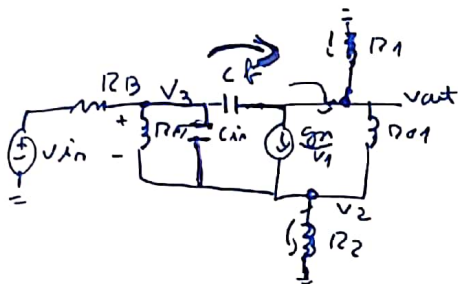

11 model

3 nodes  
 $V_{23} - V_{12} = V_1$



Input Impedance

$$\frac{V_{in}}{I_{in}} = R_B + r_{\pi} + R_2$$

Transconductance

$$I_O = g_m v_1$$

$$I_B = \frac{v_{in}}{R_B + r_{\pi} + R_2}$$

$$v_1 = I_B r_{\pi}$$

$$v_1 = \frac{v_{in}}{R_B + r_{\pi} + R_2} \times r_{\pi}$$

$$I_O = \frac{g_m r_{\pi} v_{in}}{R_B + r_{\pi} + R_2}$$

$$\frac{I_O}{v_{in}} = \frac{g_m r_{\pi}}{R_B + r_{\pi} + R_2}$$

$$v_2 = \frac{R_2 v_{in}}{R_B + r_{\pi} + R_2}$$

$$v_1 = \frac{v_{in} r_{\pi}}{R_B + r_{\pi} + R_2}$$

$$\frac{v_{out}}{r_{\pi}} + \frac{v_{out} - v_2}{R_{O1}} + g_m v_1 = 0$$

$$v_{out} \left( \frac{1}{r_{\pi}} + \frac{1}{R_{O1}} \right) + v_{in} \left( \frac{r_{\pi} g_m}{R_B + r_{\pi} + R_2} - \frac{R_2}{R_B + r_{\pi} + R_2} \right) = 0$$

$$\Delta V(1)$$

$$V_1 = V_3 - V_2$$

$$(V_3 - V_2) \left( \frac{c f_{im} \beta \beta + 1}{\beta \beta} \right) + \frac{(V_3 - V_{im})}{\beta \beta} + c f_{\beta} (V_3 - V_{out})$$

$$V_3 = \frac{V_2 \frac{c f_{im} \beta \beta + 1}{\beta \beta} + \frac{V_{im}}{\beta \beta} + V_{out} c f_{\beta}}{\frac{c f_{im} \beta \beta + 1}{\beta \beta} + \frac{(V_3 - V_{im})}{\beta \beta} + c f_{\beta} (V_3 - V_{out})}$$

$$\frac{V_2}{\beta \beta} + \frac{V_2 - V_{out}}{\beta \beta} - g_m \hat{V_1} + \overbrace{(V_2 - V_3)}^{V_1} \left( \frac{\beta \beta (c f_{im} \beta \beta + 1)}{\beta \beta} \right) = 0$$

$$V_2 = \frac{\frac{V_{out}}{\beta \beta} + g_m V_3 + V_3 \left( \frac{\beta \beta (c f_{im} \beta \beta + 1)}{\beta \beta} \right)}{\frac{1}{\beta \beta} + \frac{1}{\beta \beta} + g_m + \frac{\beta \beta c f_{\beta} \beta \beta + 1}{\beta \beta}}$$


can't reach an expression To solve

very complicated

'Approximated version'

$$\frac{I_0}{V_{in}} = \frac{g_m Z_{eq}}{r_B + r_{eq} + r_2} = G_M V_1$$
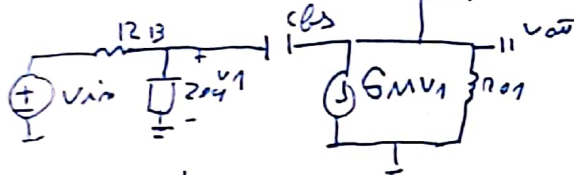
$$Z_{eq} \approx \frac{r_2}{r_2 C_{in} s + 1}$$



"new representation"  
of the circuit

Same thing as the the

CE Resistor

But new  $g_m$  is directly dependent  
On

But switch  $g_m$  with  $G_M$

The rest

Is equal to the CE stage Resistor

But with  
an  $g_m$  dependent  
on Frequency